

Title: Design & realization of flip-flop conversion

Objective:

- 1) To design & implement JK-to D ff conversion.
- 2) To design & implement D to T ff conversion.


Apparatus: Digital board, GP-4-patch cords, IC74LS74, IC74LS86, IC74LS76, IC74LS04.

Theory


concept of ff conversion.

- 1) The conversion from one type of ff to other is actually a combination of given ff & combinational circuits using gates.
- 2) The inputs to ff conversion logic are the ff data inputs & the outputs of the given ff are the desired flip-flop outputs.
- 3) The conversion logic is designed by combining the excitation tables of both flip-flops.
- 4) Then we draw k-map for each output to obtain the simplified logic expressions.


Pin diagram

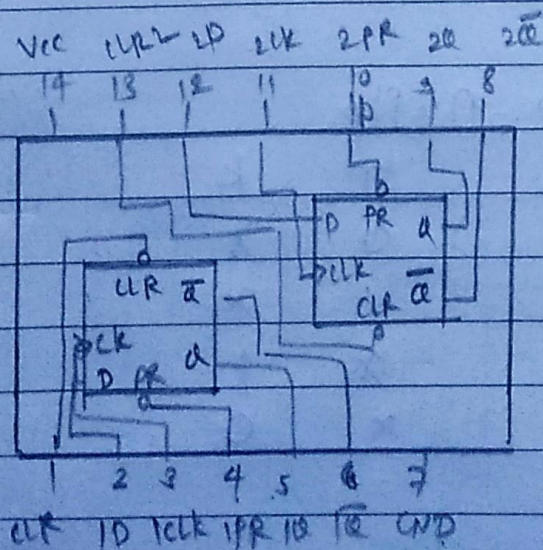

7474

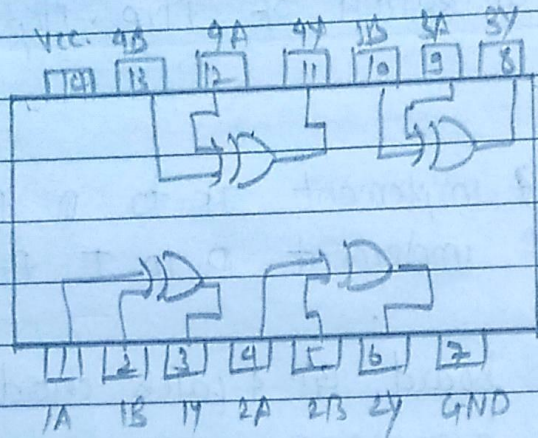

7486 pinout

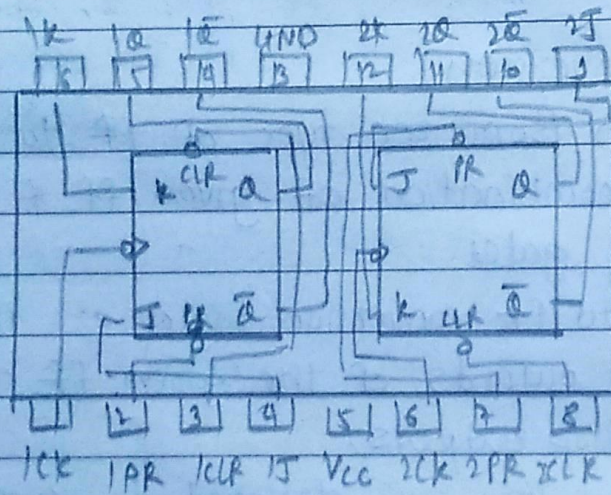

7476




Procedure

- 1> Make the connections as per the truth table of JK to D flip-flop conversion.
- 2> Make the connections as per truth table of D to T flip-flop conversion.

Design of JK to D flip-flop.

D	Q _n	Q _{n+1}	J	K
0	0	0	0	X
1	0	1	1	X
0	1	0	X	1
1	1	1	X	0


kmap simplification...

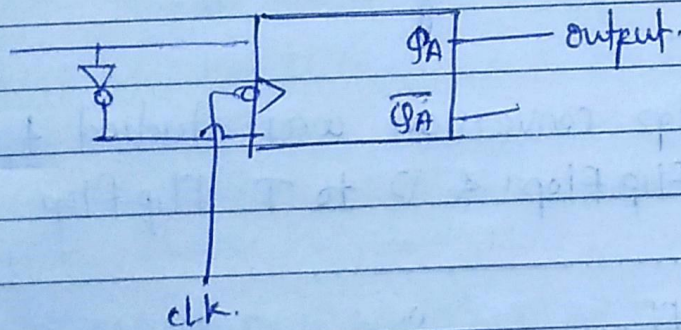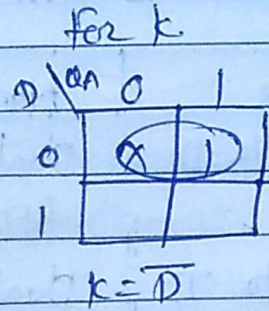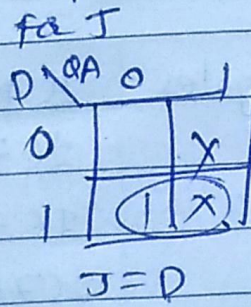


Design of D ff to T ff:

T	Q _n	Q _{n+1}	D
0	0	0	0
1	0	1	1
1	1	0	0
0	1	1	1

kmap simplification:

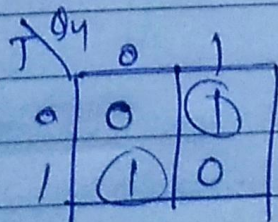

$$D = T\overline{Q_n} + TQ_n$$

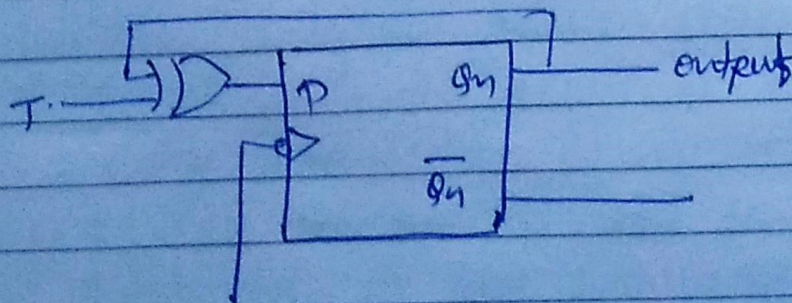

DATE PAGE NO.

Logic gates / MSI device required for implementation.

Sr No	Title	Name of IC	No. of gates	IC Number
1	Jk to D	Dual MS JK FF	1	IC 74LS76
		FF NOT	1	IC 74LS04
2	D to T	Dual D ff	1	IC 74LS74
		XOR	1	IC 74LS86

Conclusion

Concept of flip-flop conversion was studied & conversions from JK to D flip-flop & D to T flip-flop were implemented.