

Title: Sequence detector circuit.


Objective: To design & implement sequence detector for sequence 101 using JK Flip-flop.

Apparatus: Digital board, GP-4 patch-cords, IC 74LS76, IC 74LS08, IC 74LS04, IC 74LS32 & required logic gates if any.


Theory:

1. The sequence detector is synchronous FSM to detect sequence applied to the input.
2. It checks the input sequence bit by bit & moves to the next state if desired bit is obtained.
3. The o/p of the circuit is zero as long as complete sequence is not detected.
4. The o/p becomes one as soon as the complete sequence is detected at the input side.
5. The sequence detector can be implemented using JK ff.
 - (a) D ff.
6. Moore model can be used for implementation.

Pin diagram:

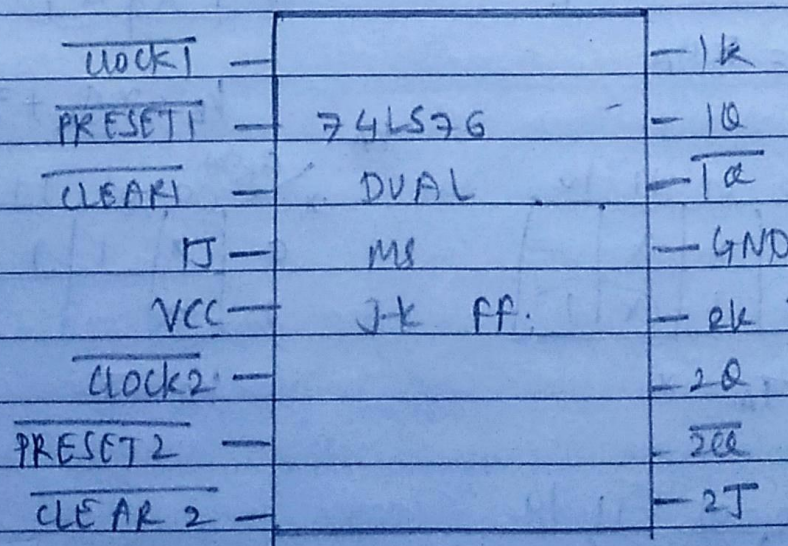

01118

 

procedure:

Make the connections as per the logic circuit of sequence detector circuit using IC 74LS76 & verify its truth table.

Design of sequence detector

X	Q _B	Q _A	Q _B ⁺	Q _A ⁺	J _B	K _B	J _A	K _A	Y
0	0	0	0	0	0	x	0	x	0
0	0	1	1	0	1	x	x	1	0
0	1	0	0	0	x	1	0	x	0
0	1	1	1	0	x	0	x	1	1
1	0	0	0	1	0	x	1	x	0
1	0	1	0	1	0	x	x	0	0
1	1	0	1	1	x	0	1	x	0
1	1	1	0	1	x	1	x	0	1

k-map: simplification

J_B x Q_B Q_A

	00	01	11	10
0	0	1	x	x
1	0	0	x	x

$$J_B = \bar{x} Q_A$$

K_B x Q_B Q_A

	00	01	11	10
0	x	x	0	1
1	x	x	1	0

$$K_B = x Q_A + \bar{x} \bar{Q}_A$$

J_A x Q_B Q_A

	00	01	11	10
0		x	x	
1	1	1	x	1

$$J_A = x$$

K_A x Q_B Q_A

	00	01	11	10
0	x	1	1	x
1	x			x


$$K_A = \bar{x}$$

Y x Q_B Q_A

	00	01	11	10
0			1	
1			1	

$$Y = Q_B Q_A$$

logic diagram

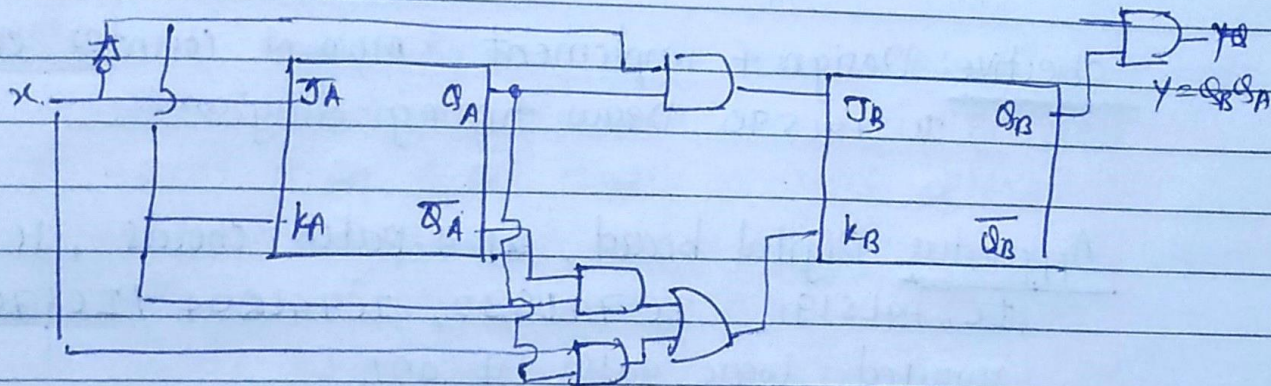

logic gates/ MSI device required for implementation:

sequence detector	IC's required	quantity	IC req.
101	NOT	2	IC7404
	AND	4	IC7408
	OR	1	
	DUAL MS JK FF	2	IC7476-1 no.

Conclusion

concept of sequence detector is studied & implemented